


Another super computer for INDIA

Annapurna is the yet another Super computer of India which is developed by Institute of Mathematical Sciences in Chennai.


Smartphone Asia

It is speculated that by the year 2015 half of the cellphone sales will consist of smartphones in Asia with an estimated figure of 477 million units to be sold

DIY

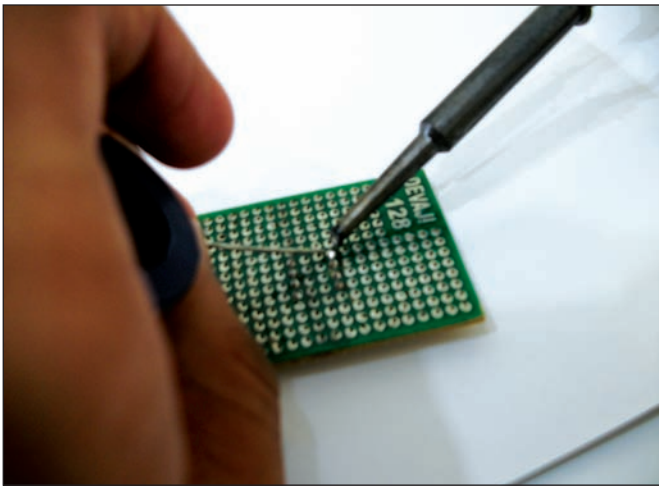

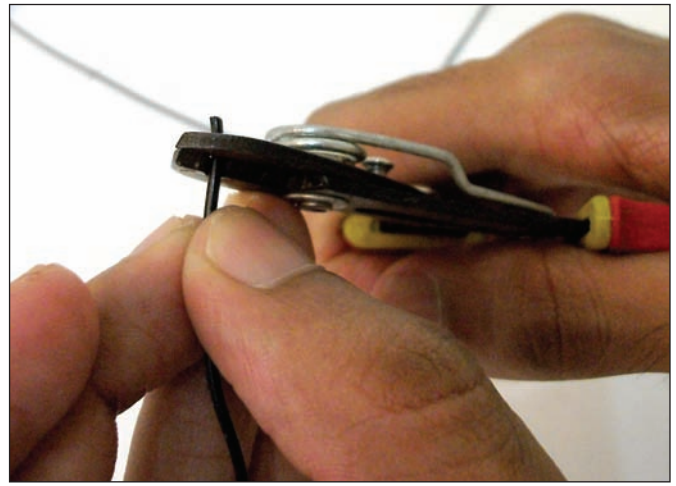Be careful with your components. Overheating them can damage them permanently




The right tools will save a lot of time


We tried it near a dog. Although it did run away, we're still trying to figure out whether it was because of the circuit or it seeing some alien device being brought towards it! First, gather your components together. Clean the surfaces to get rid of oxidised surfaces. Clean the leads using a blade. Insert the IC, especially if you are using a small piece of board as we did. This way you get to know the approximate area you would

need. Use an IC base in case you are not used to soldering so that you don't damage the IC.

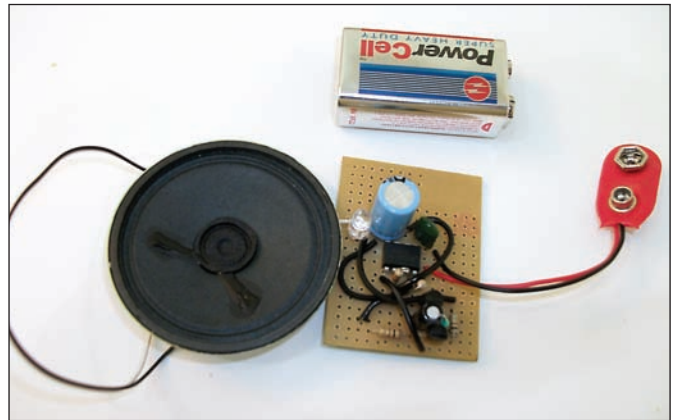Next insert the resistors in to the PCB according to the circuit diagram. Lastly insert the capacitors, LED and speaker. Connect the battery snap. You should now have a working pest repellent. Try it out by switching it on. The LED should turn on indicating a working circuit. And you're ready to shoo pests away!



Use a wire stripper to strip wires

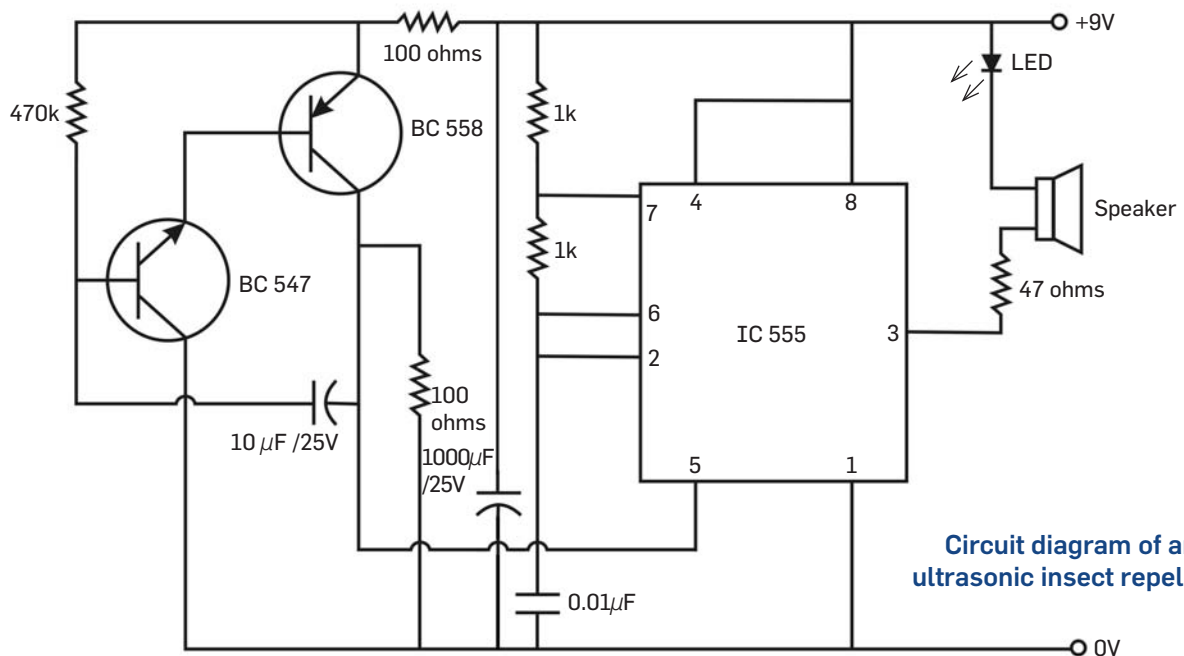

Circuit diagram of an ultrasonic insect repellent