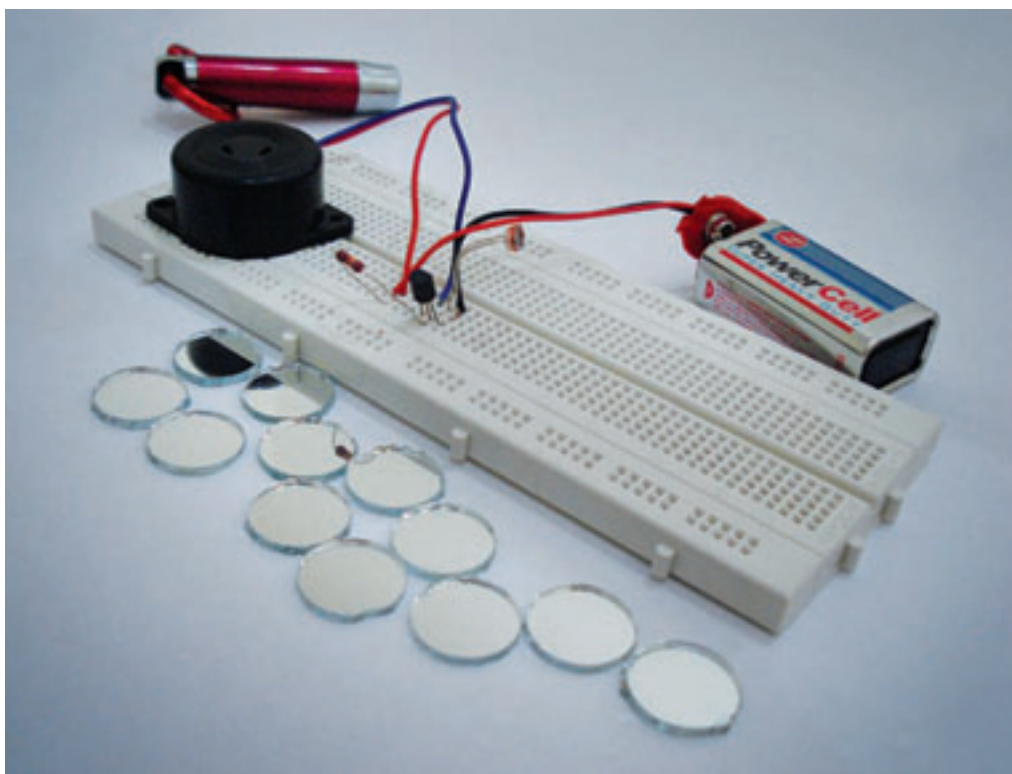


Norton reports

A study conducted by Norton reports that nearly two-thirds of internet users globally and almost three-quarters in the U.S. have fallen victim to cybercrime, with even worse numbers in China, where 83 per cent have been hacked

High-Def Hacked

HDCP (High-bandwidth Digital Content Protection) keeps devices such as Blu-ray players and HD set-top boxes protected, has been hacked



Secure your belongings, the smarter way

With every instance of shopping sprees indulge in, there is a higher possibility of theft that haunts us. We show you how you could safeguard your possessions in just ₹100!

Nash David
nash.david@thinkdigit.com

If you've seen the 1999 Hollywood movie Entrapment starring Catherine Zeta-Jones, you'll know exactly what we're talking about here. No we're not interested in the attractive female secret agents steering through laser controlled security systems! We're excited about the

technology that goes along with it. We're talking about you being able to safeguard your valuables, so that you can enjoy a good night's sleep. If someone wants to steal from you, they should at least have a tough time getting past your security shield.

This is how it works

The working principle of the circuit we're building this

month is really simple. What is critical is the set up. Although you'll find several versions and alternatives available to achieve the same ulterior motive, we're presenting you this circuit purely for its simplicity and efficiency. It's so simple you can build it even if you don't know anything about electronics. To take you through its working, we use one of those laser key chains that we're used to seeing

while growing up. You use one of the laser pointers and direct its beam at the laser receiver we're building.

The basic component that detects the laser is a simple light dependent resistor (LDR). We discussed about electronic components in this month's webinar on our website at www.thinkdigit.com/webinars.php. If you read through our presentation, you'll get a better understanding of what a light dependent resistor is.

The laser beam should be incident on the LDR during normal operation of the circuit. In the event of an intrusion, the laser network that you'll create using tiny mirrors is obstructed. The LDR detects this obstruction and in conjunction with the transistor interprets it as a change in state. The resultant change in electrical signals triggers the buzzer to alert anyone around you of the ongoing theft attempt. Vigilant neighbours and friends are all you need to foil the intrusion attempt.

Identifying your components

The picture alongside gives you a glimpse of the components you are going to use for this DIY. The buzzer has two wires – one red and the other blue. Connect the red wire to the positive terminal, and the

What you will need:

Transistor 2N3904 – 1 no.
Capacitor: 1000uF – 1 no.
Laser pointer
LDR
Resistor: 10K
Breadboard
Piezo buzzer (3 – 12 V)
9V battery – 1 no.
Battery snap
A pack of tiny mirrors, commonly available with tailoring shops specialising in embroidery work.
Fevikwik for fixing your mirror pieces