


## Google Apps doubly secure

Google Apps is launching two-factor verification, allowing the capability to verify a person's identity with a code sent to the user's mobile device

## Phishing galore

A Spanish security firm called PandaLabs estimates 57,000 sites designed to look like other popular sites go up on the web each week. These phishers try to trick users into handing over personal details

DIY

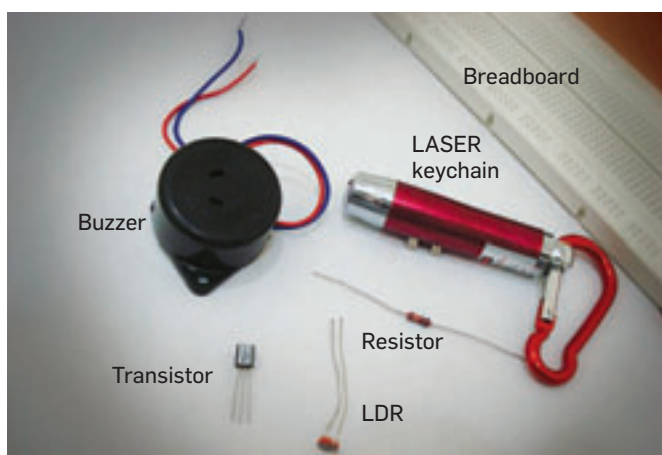

Components for your new security system




The 10 kilo ohm resistor is connected to the base of the transistor

other wire to the negative terminal. The transistor is an NPN transistor and has three terminals known as collector, base and emitter. You can identify the terminals from the photo or you can also refer to a datasheet. If you place the circular side of the case to the left (resembling a C), with the flat side to the right and the terminal facing down, then the terminal towards you is the emitter. The terminal in the middle is the base and the terminal on top is the collector. ie. The terminal on top of your C is the collector, the middle is the base and the terminal on the base of your C is the emitter. The LDR or light dependent resistor has two terminals with a wavy line on it.
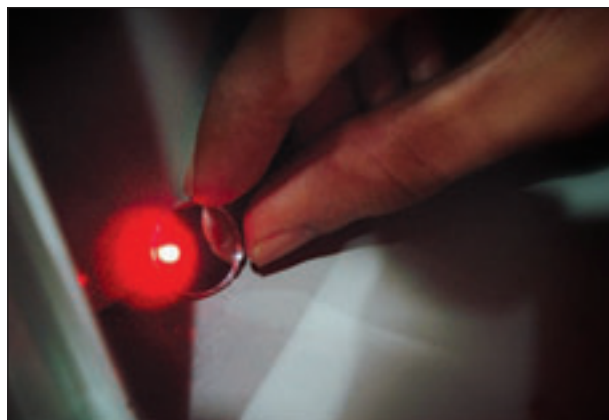
## Connecting the components together

You can start with a breadboard to test this project so that you don't get frustrated if it doesn't work. As you can see, the circuit is very small and simple. With just three components in it, you should be able to get it without any prior knowledge of electronics. To start, place the transistor on the breadboard, as shown in the photo – the flat side facing you. If you'd




Create a mesh around your belongings using LASER and mirrors

try and recollect now, the terminals from left to right are emitter, base and collector.

Connect the LDR between the two terminals to the left of



You can now relax

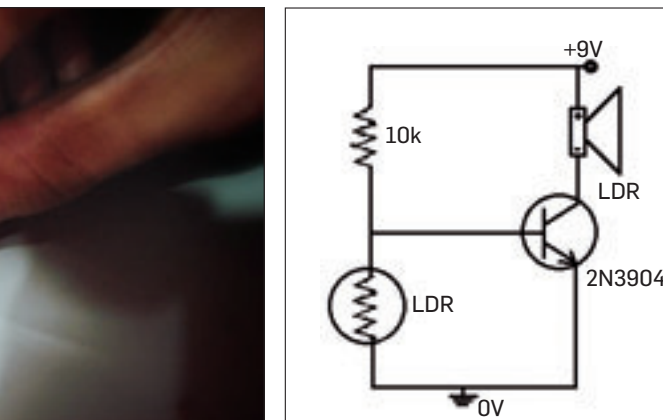

Just four components as you can see in the circuit diagram

the transistor (base and emitter). Connect the buzzer between the third terminal of the transistor (collector) and a new point X on the board. To this point, connect one terminal of the resistor (10K). The other terminal of the resistor connects to the collector of the transistor.

To the common point between the resistor and the red wire of the buzzer, connect the red wire (positive) of the battery. Similarly, connect the black wire (negative) of the battery to the emitter of the transistor.

## You're done...really!

Believe it or not, half your work is done. Although, by way of constructing the circuit you've completed your

job. Now, you are left with craft work literally. Strategically place the mirrors such that they are not easily visible and create a mesh of LASER around your valuables. We prefer mirrors because other reflective materials tend to dissipate or distort the beams, thereby causing problems with the sensitivity of the circuit. There's no limit to the network you could form by the mirrors. All you need to do is ensure that the beam finally falls on the LDR in normal circumstances. This way your buzzer will be off in normal state. If you want a more permanent solution, solder the components together and keep the LDR concealed so that the LASER beam is not seen.