

HTC doubles profit

Taiwanese phonemaker HTC's earnings report shows their profits have doubled thanks to Android sales



Internet Explorer falls!

Statcounter revealed that last month, the number of people using IE fell below 50%


DIY

Nash David

nash.david@thinkdigit.com

When we've bought ourselves a brand new computer, we tend to take good care of it, ensuring temperatures don't rise beyond the recommended level. Sooner or later we tend to take our computing marvel for granted, such as much as we can from it, till it finally comes to a standstill – refusing to budge this time!

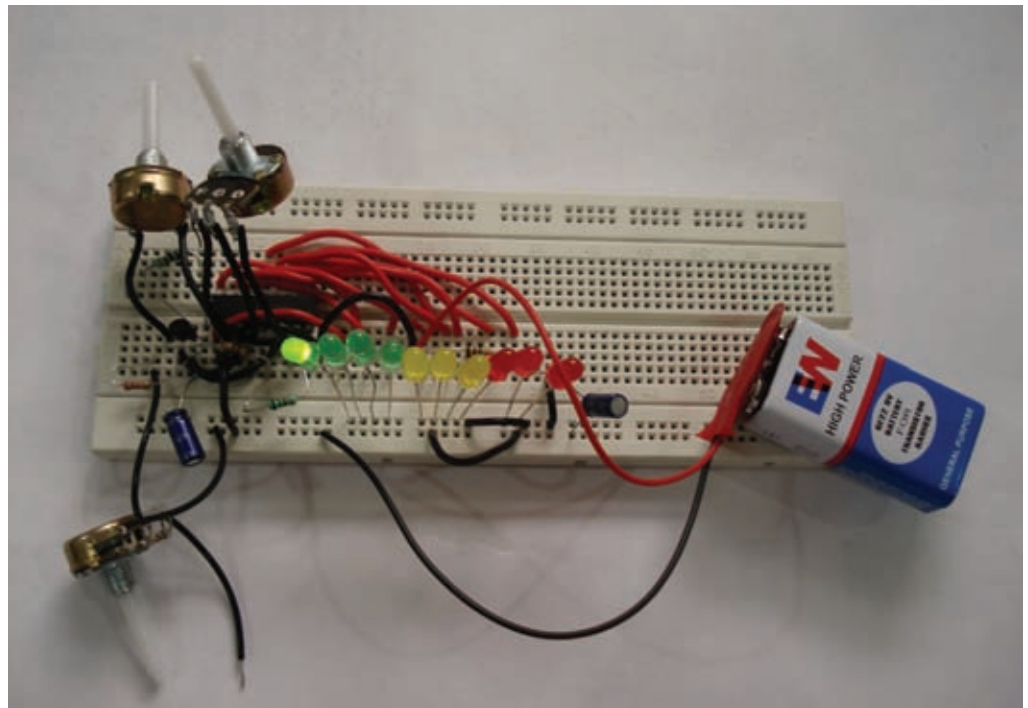All of this could be avoided with corrective and preventive measures taken before hand. For one, most people find it inconvenient to repeatedly go to the BIOS of their system to check the processor and cabinet



Each LED glows as the temperature increases

PC temperature monitor

This month, we look at an electronic circuit that would help you monitor your PC's temperature. All you need to do is build this circuit and place it near your processor. Depending on the temperature, the LED array would light up indicating a rising temperature

temperature. Again, installing a software purely for diagnostics is unfortunately perceived

as a waste of system resources. Popularly, users would rather have the system informing

them of critical milestones.


What to expect

The primary objective of this circuit is to inform you of the temperature of its vicinity, so that you can take precautionary measures. IC LM35DZ is a precision Celsius temperature sensor. It converts ambient temperature into an equivalent analogue voltage. This analogue signal is translated into an equivalent bar graph by the bar/dot graph driver IC LM3914. Ten LEDs form the bar graph. We recommend using three colours – green, yellow and red to depict the bar graph. Green indicating

normal operational temperature, yellow indicating the warming up phase and red approaching breakdown point.

Assembly

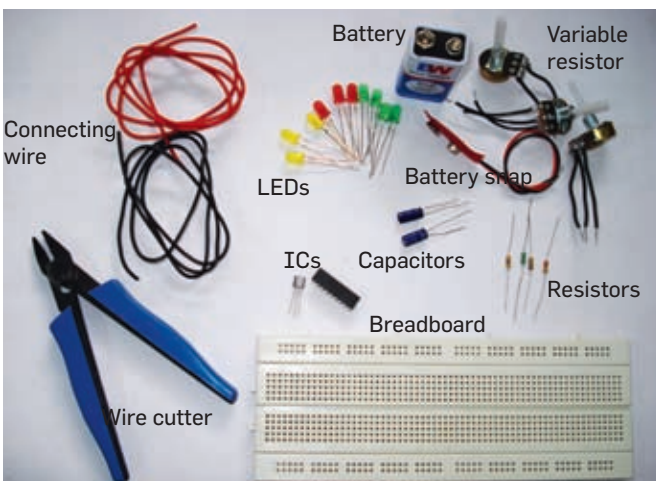Refer to the circuit diagram. Begin with temperature sensor LM35DZ. If you look at the bottom side with the pins facing you and the flat side facing up, then the terminals



Make sure you have all the components before you begin building

What you will need

Capacitors

- C1 - 1uF / 25V Electrolytic
- C2 - 10uF / 25V Electrolytic

Resistors

- R1 - 2.2k
- R2, R5, R7 - 1k variable resistor
- R3 - 1k
- R4 - 1.5k
- R6 - 470 ohms
- R8 - 100 ohms

Diodes

- D1-D10 - LEDs

ICs

- U1 - LM35DZ Precision Centigrade Temperature sensor
- U2 - LM3914 Bar/Dot graph driver IC

Miscellaneous

- Breadboard, connecting wire, wire cutter/stripper, 9V battery, battery snap