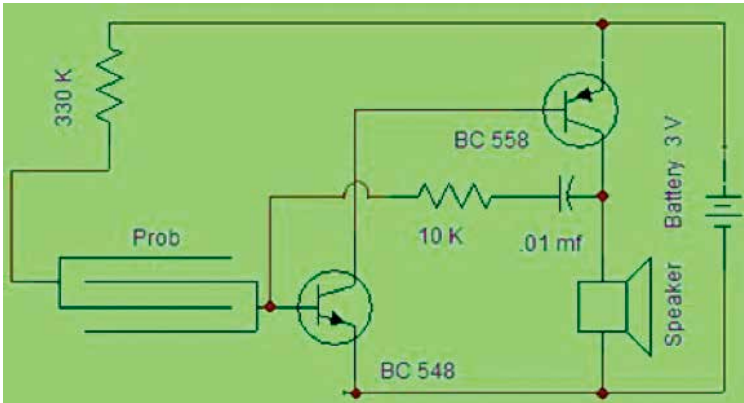





<https://www.elprocus.com>

able objects that could be spoilt by rain. The components required for this circuit are the following - Probes, 10K and 330K resistors, BC 548 and BC 558 transistors, 3V battery, one mf capacitor, and a speaker.

When the rainwater comes in contact with the probe in the given circuit, the current flows in the circuit to enable Q1, NPN transistor which in turn makes Q2 (PNP) transistor active. When Q2 starts conducting, the current flows through the speakers which start buzzing. This cycle is repeated until the probe remains in contact with water.

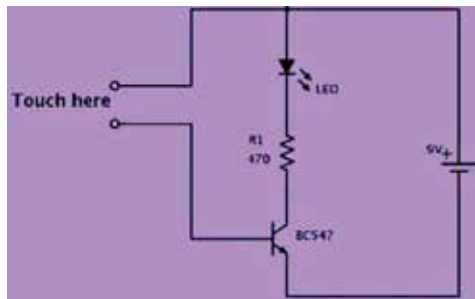2. Touch Sensor Circuit

The touch sensor circuit can be built using three main components which are a resistor, a transistor, and an LED (Light Emitting Diode). Here the LED and the resistor are connected in series with the positive supply and then to the collector terminal of the transistor. Select a resistor and set the current of LED to 20mA, then supply the connection to the exposed ends; one goes to the positive end while the other goes to the base terminal of the transistor. On touching these two wires with your finger, the LED will light up.



<https://www.elprocus.com>