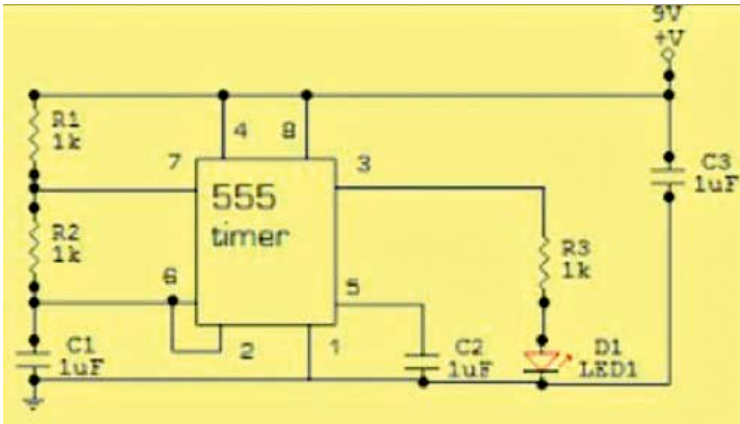


3. LED Flasher Circuit

Starting from the left and going on to the right of the circuit, the capacitor and the two transistors used in the circuit are responsible for setting the time that it takes to switch LED ON and OFF. The IC 555 is used to determine the



<https://www.elprocus.com>

amount of time the LED has been ON or OFF, though it is a difficult circuit from inside, it readily available as an IC in the market. The two capacitors are placed at the right side of the timer, and these are required for the capacitor to work properly, while the resistor is used so that excessive current doesn't enter the LED and damage it.

Understanding how to Read Circuit Notations

Circuit Diagrams are always important, especially when dealing with complex circuits such as the ones you'll be dealing with when working on PCBs such as Raspberry Pi and Arduino. To be able to understand the circuit drawn on paper and to implement it, the person dealing with it must, without a doubt, know how to read the Circuit Diagram.

After going through the basics of Understanding PCBs, forms of communications, and going through some basic circuits, this last section of the chapter will focus on guiding the readers on how to read circuit notations.

Schematic Symbols Part 1- Basics

Below given are the most basic standardised symbols for various components, read and understand them carefully.