

advanced automation along with Amazon Alexa and IFTTT. You can get this system at value, offering a scalable self-installation system.

DIY - Simple Security Alarm Circuit Working And Applications

A circuit consists of various components like resistors, transistors, capacitors, inductors, and diodes. All these components are connected with the help of conducting wires so that current can flow through the circuit.

There are two types of electronic circuits:

Analog circuits:

These electronic circuits are basically circuits where the current or the voltage may vary accordingly. The analog circuits can be constructed in two ways either with the series connection or with the parallel connection. When the circuits are connected in a series connection what happens is that all the components in the circuit are connected to the same current or you can say in the series connection the same current flows throughout the circuit. So, if any part in the circuit has any problem the whole circuit has the same impact.

For example, the decoration LED lights are actually connected in a series connection, so whenever one of them goes out, then they all go out at the same time.

There is another type of connection, as discussed above, the parallel connection. Here, every component experiences the same voltage, but the current flowing in the circuit may vary on the basis of the resistance of the various components inside the circuit. The components that are used in the analog circuits are the wires, resistors, capacitors, inductors, diodes, and transistors.

Digital circuits:

The various components of the circuit:

- 1) Wires:** This is basically a cylindrical collection of coiled metal that can be kept as a coil. They are basically used to bear the capacity or the high power of the electricity and also can be used for telecommunication signals. Wires usually come in a cross-section pattern, but it can also be designed in other patterns based on the efficiency of the circuit or also for certain decorative purposes. They can be designed in square, hexagonal, flattened rectangular and other patterns, as required. There are also certain different types of wire-like- The hook-up wire, which