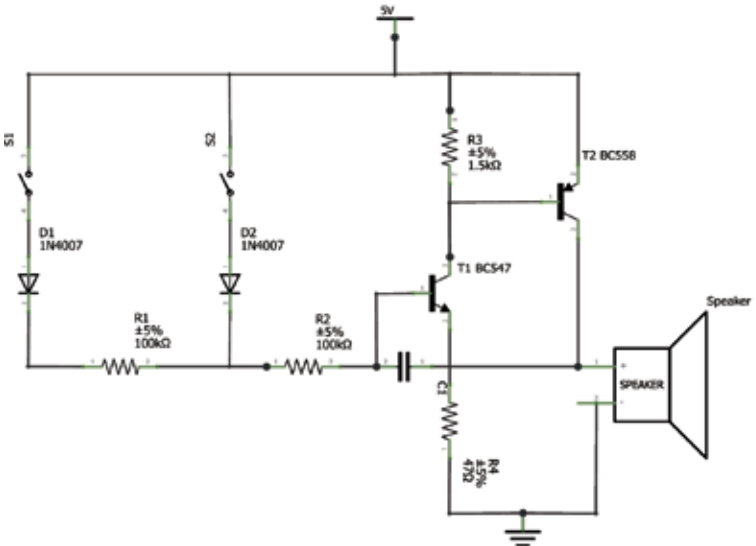


just need to place your circuit in that area, and when anyone tries to open your locker or possibly, wanders nearby that area, then it detects the signal and switches on its alarm sound to give you an alert that your secure safe has been compromised.

The main objective of this circuit is that it can work in two places at the same time and can create two alarm sounds when safety is compromised. The circuit components that are used in this alarm circuit.

- Resistor
- R1, R2 (100K)-2
- R3 (1.2K)-1
- R4 (47E)-1
- T1 (BC547)- 1
- T2 (BC558)- 1
- D1, D2 (1N4007)- 2
- S1, S2- 2
- Speaker- 1



How it works

The circuit is fairly simple in operation. You have two switches S1 and S2 which are both connected to their individual resistors. There are also two diodes D1 and D2 present to ensure current only flows in one direction in