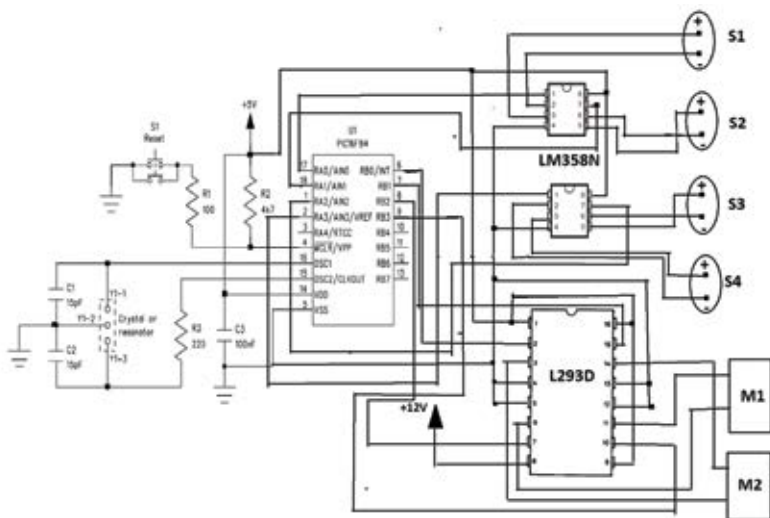


## 6

input to sensors and PORT B as output to motors. Though we are going to use two sensors, but in the following schematics I have given the wiring for four sensors, to leave scope for improvement. Once you have successfully made a line follower, you can make a more advanced line follower which can respond to intersections and acute angles, and for that purpose you would



need more than two sensors. So it's better to include four sensors now only, so that you don't need to make the circuit again when you decide on making the advanced line follower. However for now, we will only use S1 and S2 as left sensor and right sensor respectively. S1 will give input to pin AO (called RAO) and S2 will give input to pin A1 (called RA1). The output to the left motor is given by pins RB3 and RB2, and the output to right motor is given by pins RB1 and RB0. Both these outputs are first fed through L293D motor driver, which provides necessary amplification required to driver a 12V DC motor. 