
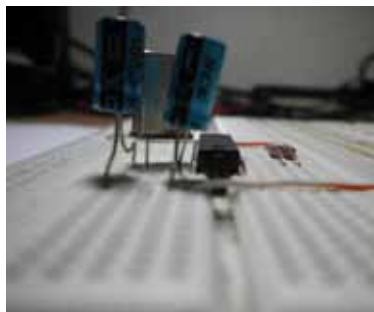


7 Making the Circuit

We would be building the circuit on breadboard. It would be good if we make the circuit on two breadboards joined together so that we may have enough space for wiring every component.

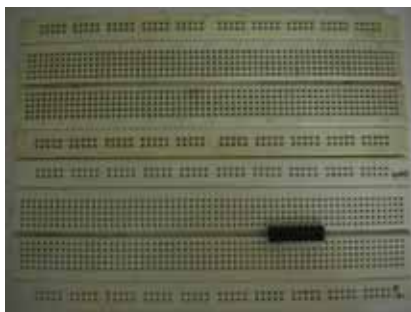Two breadboards joined together and a PIC16F84 placed on them is shown in the following figure:



The next step is to make the clock circuit for the PIC using a 4 MHz oscillator. It is shown below:

The next step would be to make the voltage regulator circuit to convert 12 volt input from battery to 5V. This circuit is built alongside the PIC Circuit, and the PIC is powered using this circuit.

In the next step the motor driver IC L293D and the Opamps LM358N are placed. Also Opamp is powered.

Finally all connections except those for sensors and motors are made and we get the following circuit:

