
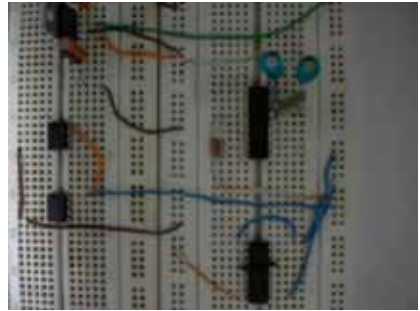
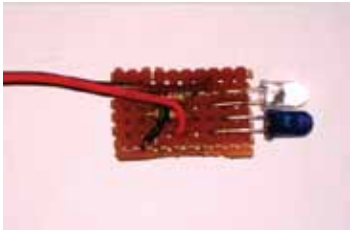


7 Making the Circuit

Build your own robot

The connections for sensors and motors will be done after the breadboard is mounted on robot body.

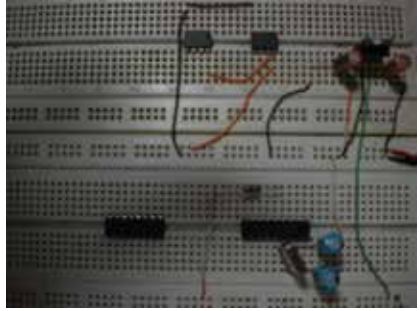For making the sensor, you will have to do soldering because breadboards are too large for a small sensor and it is difficult to place a breadboard at the position where the sensor is usually



mounted. So, if you don't know how to solder, you can take help of someone who knows it. Following is the snapshot of the sensor I made on a PCB based on the same circuit diagram for a sensor given earlier in chapter 'Designing the circuit'. 