



Facebook random similarities

Facebook is testing feature that'll call out the things users might have in common with random strangers. <https://digit.in/sep18-30-1>



Windows 95 app

Slack developer Felix Rieseberg created an app that allows Windows 95 on modern operating systems. <https://digit.in/sep18-30-2>

SLAYER EXCITER

Get your voodoo game on with this simple and sage wireless power transmission project.

Mithun Mohandas | mithun@digit.in



Often described as a Tesla Coil, this variant is actually called Slayer Exciter and it was conceptualised by a YouTuber by the name of GBLuer. It's a very simple circuit that is built using commonly found electronic components and there have been many variants developed since GBLuer's initial experiment with varying results. Some are powerful enough to produce small electric arcs but the one we're going to be building today is a much safer alternative. It produces really high voltage but carries negligible current so there isn't a risk to life, if you're worried about that. The only caveat is that you do not deviate from the circuit provided.

alised by a YouTuber by the name of GBLuer. It's a very simple circuit that is built using commonly found electronic components and there have been many variants developed since GBLuer's initial experiment with varying results. Some are powerful enough to produce small electric arcs but the one we're going to be building today is a much safer alternative. It produces really high voltage but carries negligible current so there isn't a risk to life, if you're worried about that. The only caveat is that you do not deviate from the circuit provided.

THINGS YOU'LL NEED

Given the simple nature of this Slayer Exciter circuit, you do not need a lot of expensive parts. In fact, most of the parts can be found at your local hardware store. Here's the entire list.

- 2N2222 Transistor
- 22K Ohm Resistor
- 45 meters of 30 AWG Magnet wire
- 1 meter of 20 AWG Magnet wire or any insulated single strand copper

- wire will do
- Breadboard
- 3 or 5 mm LED
- 9 V Battery
- Foot-long plastic tube of 1-inch diameter
- Aluminium Foil (Enough to make a 2-inch diameter ball)
- Multimeter
- Transparent nail polish (Optional)
- Insulation tape
- Switch (Can be a push-to-on)
- Tools and connecting wires
- CFL bulb to test

The 2N2222 transistor can be substituted with any other transistor as long as the Vce and hfe values match. It has to be an NPN transistor with more than 50V for the vce and more than 60 hfe. Search for the datasheet of the transistor and you'll see these values. You can use 2N5550 as an alternative. The package of the transistor doesn't matter. If your resistor value drops too low then you'll be driving the circuit stronger and that will cause the transistor to heat up a bit.

The longer piece of magnet wire need not necessarily be of 30 AWG thickness. It can be whatever you want, it's just that 30 AWG allows us to pack a lot of coils in the same space as compared to using a thicker wire. What you need to ensure is that the magnet wire (or enamelled wire) is properly handled,

else you risk stripping the enamelling and you might short your coil, thereby, reducing its efficacy.

STEP 1 - MAKING THE COIL

The most time-consuming step in the Slayer Exciter circuit is making the coil. Take the 30 AWG magnet wire or enamelled wire and affix it to one end of the plastic tube. Now start coiling the enamelled wire onto the plastic tube. Ensure that the wires don't overlap and you have a neat and clean

coil running all the way to the other end. Use the nail polish as a glue to keep the wire from uncoiling off the tube. We didn't use any but there were instances when we lost our grip while making the coil that made us regret that.

Once you've got the entire plastic tube covered with the magnet wire, you should have the two ends of the wire on either end of the tube. Take these ends and strip the enamelling off these ends. On one end, i.e. the top side, you need to have a load. The objective here is to increase the area occupied by this positive end. We used the aluminium foil and crumpled it into a ball shape which was then connected to one end of the 30 AWG magnet wire and glued to the top of the plastic tube. This is called the secondary coil. The next step is to make



The secondary coil



Secondary with primary wound on it